

Fig. 4. The addition of negative feedback to the amplifier of fig. 1.  
See pages 8 and 9 for component values.

### A 50W ULTRA LINEAR AMPLIFIER

When the maximum output is required from a pair of KT66 valves they may be used with fixed bias in the ultra-linear circuit. The operating conditions are given below and the recommended circuit is shown in fig. 5.

Per Pair of Valves	Quiescent	Max. Signal	
$V_{a,g2}$	525	500	V
$I_{a+g2}$	70	160	mA
$V_{g1}$	-50/-65	-50/-65	V
$\dagger R_{L(a-a)}$	—	8	k $\Omega$
$P_{out}$	—	50	W
*D	—	2	%
$P_{a+g2}$ (per valve)	18	15	W
$z_{out}$	—	6	k $\Omega$
$V_{in(g1-g1)}$ (rms)	—	90	V
$V_{in}$ (to amplifier in fig. 5)	—	2.5	V

$\dagger$ An output transformer having a ratio of 6 : 1 would be suitable for 105V output, 225 $\Omega$ .

\*The distortion will vary from 1% to 3% with different valves. The performance is displayed graphically in figs. 7 and 8.

#### Circuit Notes.

The two KT66 valves are set to a similar quiescent current, which may be between 30 and 40mA, using the meter M and the meter shunts R46, R47. A negative bias voltage range of 50 to 65 is provided by the controls R53, R54. A quiescent current below 30mA will increase the distortion.

The bias voltage is derived from a U50 connected to the 600-0-600V transformer via the capacitors C42, C43. The resistors R55, R56, R57, R58, not only smooth the supply in conjunction with C44 but also reduce the voltage to the appropriate value. The resistors R52 to R58, associated with the bias supply, are generously rated to maintain a stable voltage.

R64 is adjusted, at about 90% of full output, to give equal cathode currents in the two output valves. It is capable of compensating for inequality of output from the driver stage and also for variations between the two output valves. When the two cathode currents are equal the distortion is at a minimum.

# KT66 CIRCUIT SUPPLEMENT

The anode supply is provided with an inductance filter L1, C31, C32. Due to the large variation in current with input signal the effective capacitance of C31, C32 has been made 80 $\mu$ F. The working voltage is excessive for a single electrolytic and C31, C32 are, therefore, connected in series to give a rated voltage of 900. This single section filter provides a ripple-free anode current. If a lower capacitance were used in place of C31, C32, an additional filter section would be required to reduce the ripple to a reasonable value, and the lower capacitance would be incapable of supplying the peak current required by a transient input signal.

At lower anode voltages the following results are obtainable. No circuit modifications are needed, the bias supply being a function of the anode voltage.

DC voltage	350	425	V
Quiescent current	25+25	30+30	mA
Max. signal current	55+55	65+65	mA
Power output	20	30	W
Anode to anode load	8	8	k $\Omega$

The value of the components C40, C41, C45 and R59 will depend to some extent on the output transformer. R59 and C45 are optional and are used to suppress ringing. The most satisfactory method of selecting the value of these four components is by the use of a square wave generator, but an audio oscillator extending to, say, 50kc/s may be used to detect a peak in the supersonic region. C40 and C41 may be unnecessary with some types of transformer.

With the transformer used, the values shown gave a fall in output of 3db at 18-20kc/s with a load resistance of 15 $\Omega$ .

### Protection Against Bias Failure.

In common with other amplifiers which derive the bias potential from a separate supply instead of a cathode resistor, the 50W amplifier is rendered inoperative should the bias supply fail. Furthermore, the KT66 anode current would rise to an excessive value. The U50 is run at a very low anode current, a few milliamperes, and will, of course, have a long life.

A simple device which permits the amplifier to function with cathode bias in case of failure of the bias supply is shown in fig. 6. A triode, which could be one half of a B65 substituted for the L63 in the first stage, is connected in series with a relay across the 500V supply. The grid is taken to the bias supply. Normally the anode current is cut off and the relay short-circuits the resistor R60 connected in the cathode circuit of the KT66 valves. Should the bias fail, the relay will be energised, the relay contacts will open and the bias resistor R60 will allow the amplifier to function at about half maximum output.

## COMPONENT VALUES

### RESISTORS

(0.25W, 20% unless otherwise shown)

R1	500k $\Omega$		
R2	750 $\Omega$		
R3	33k $\Omega$	1W	10%
R4	33k $\Omega$	1W	10%
R5	270k $\Omega$	} matched to 5%	
R6	270k $\Omega$		
R7	270k $\Omega$		10%
R8	750 $\Omega$		10%
R9	33k $\Omega$	1W	10%
R10	33k $\Omega$	1W	10%
R11	560 $\Omega$	5W w.w.	5%
R12	560 $\Omega$	5W w.w.	5%
R13	270k $\Omega$		10%
R14	270k $\Omega$		10%
R15	10k $\Omega$		
R16	10k $\Omega$		
R17	220 $\Omega$		
R18	220 $\Omega$		
R19	10k $\Omega$	0.5W	
R20	5.6k $\Omega$	1W	
R21	500k $\Omega$		
R22	750 $\Omega$		
R23	750 $\Omega$		

## CIRCUIT SUPPLEMENT **KT66**

R24 } R25 }	sec p. 3		
R31	1M $\Omega$		
R32	33k $\Omega$	0.5W } matched to	5%
R33	33k $\Omega$	0.5W }	
R34	1.5k $\Omega$		
R35	1k $\Omega$		
R36	22k $\Omega$	0.5W	
R37	1M $\Omega$		
R38	1M $\Omega$		
R39	47k $\Omega$	1W	10%
R40	47k $\Omega$	1W	10%
R41	150k $\Omega$		10%
R42	150k $\Omega$		10%
R43	10k $\Omega$	1W	10%
R44	10k $\Omega$		
R45	10k $\Omega$		
R46 } R47 }	Meter shunts		
R48	10 $\Omega$		
R49	10 $\Omega$		
R50	100 $\Omega$		
R51	100k $\Omega$	1W	10%
R52 (see fig. 6)	100k $\Omega$	1W	10%
R53	22k $\Omega$	1W	10%
R54	20k $\Omega$	w.w.	
R55	20k $\Omega$	w.w.	
R56	220k $\Omega$	1W	10%
R57	220k $\Omega$	1W	10%
R58	220k $\Omega$	1W	10%
R59	220k $\Omega$	1W	10%
R60 (see fig. 6)	330 $\Omega$	5W w.w.	10%
R61 (see fig. 6)	6.6 k $\Omega$	0.5W	10%
R62	15k $\Omega$	0.5W	10%
R63	0.65 $\Omega$	5W	
R64	20k $\Omega$		
<b>CAPACITORS</b>			
C1	0.01 $\mu$ F	350V	
C2	50 $\mu$ F	12V	Electrolytic
C3	0.1 $\mu$ F	500V	
C4	0.1 $\mu$ F	500V	
C5	100pF	250V	
C6	100pF	250V	
C7	8 $\mu$ F	450V	Electrolytic
C8	8 $\mu$ F	450V	Electrolytic
C9	0.02 $\mu$ F	500V	
C10	0.02 $\mu$ F	500V	
C11	50 $\mu$ F	50V	Electrolytic
C12	50 $\mu$ F	50V	Electrolytic
C13	2000pF	500V	
C14	2000pF	500V	
C15	8 $\mu$ F	450V	Electrolytic
C16	8 $\mu$ F	450V	Electrolytic
C21	0.01 $\mu$ F	350V	
C22	50 $\mu$ F	12V	Electrolytic
C23	50 $\mu$ F	12V	Electrolytic
C31	160 $\mu$ F	450V	Electrolytic
C32	160 $\mu$ F	450V	
C33	8 $\mu$ F	450V	
C34	8 $\mu$ F	450V	
C35	0.01 $\mu$ F	350V	
C36	0.01 $\mu$ F	500V	
C37	0.01 $\mu$ F	500V	
C38	0.05 $\mu$ F	750V	
C39	0.05 $\mu$ F	750V	
C40	0.001 $\mu$ F	300V AC	
C41	0.001 $\mu$ F	300V AC	
C42	0.025 $\mu$ F	600V AC	
C43	0.025 $\mu$ F	600V AC	
C44	4 $\mu$ F	200V	
C45	0.001 $\mu$ F	440V AC	

# KT66 CIRCUIT SUPPLEMENT

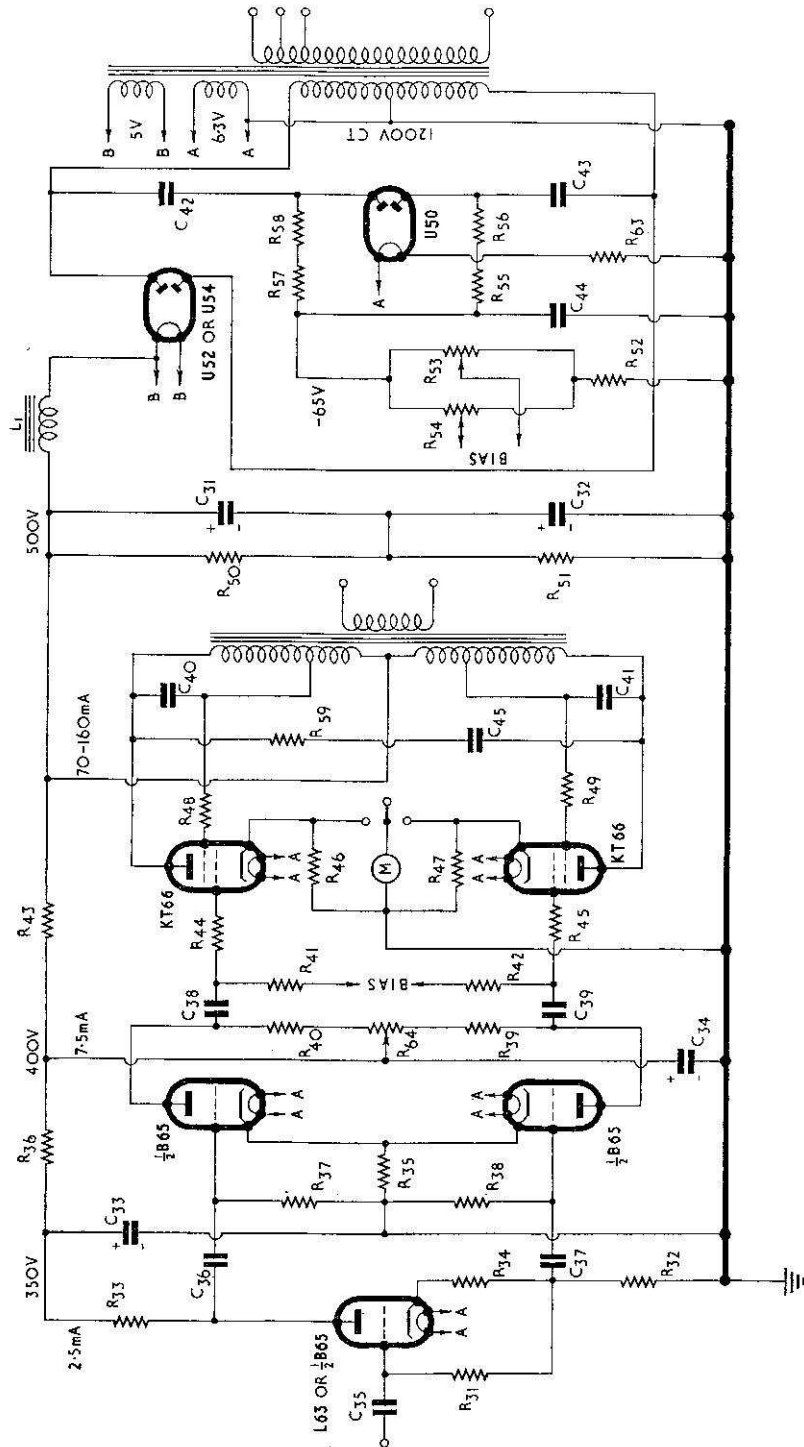


Fig. 5. A 50W ultra linear amplifier. See pages 8 and 9 for component values.

# CIRCUIT SUPPLEMENT **KT66**

Fig. 6. This circuit may be added to the 50W amplifier to protect the KT66 valves in the event of bias failure. The resistor R60, normally short-circuited by the relay, provides an emergency cathode bias. R61 and R62 replace R52.

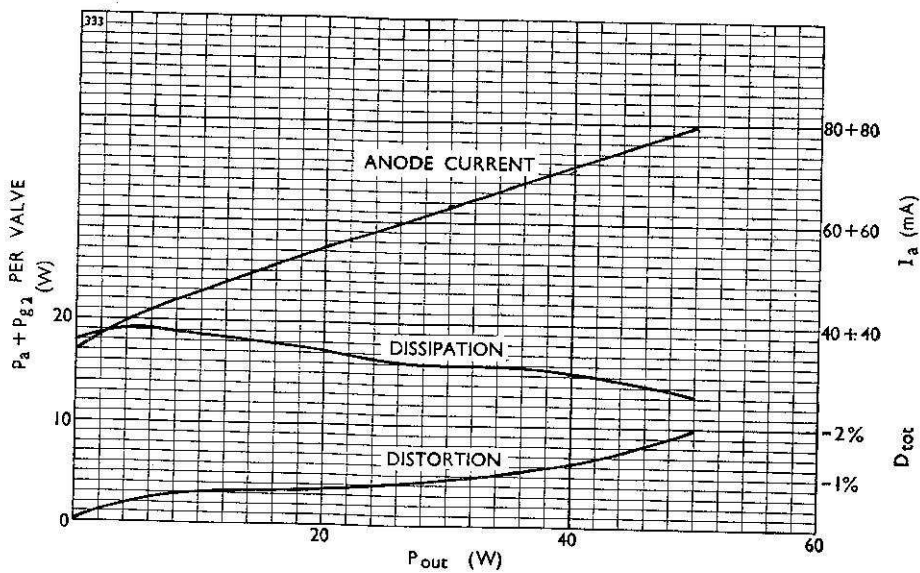
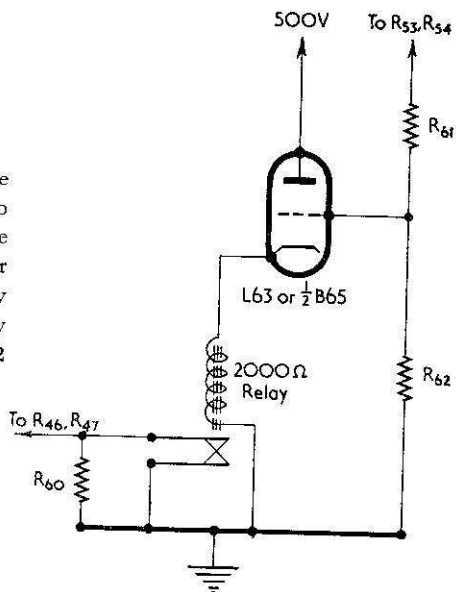


Fig. 7.

# KT66 CIRCUIT SUPPLEMENT

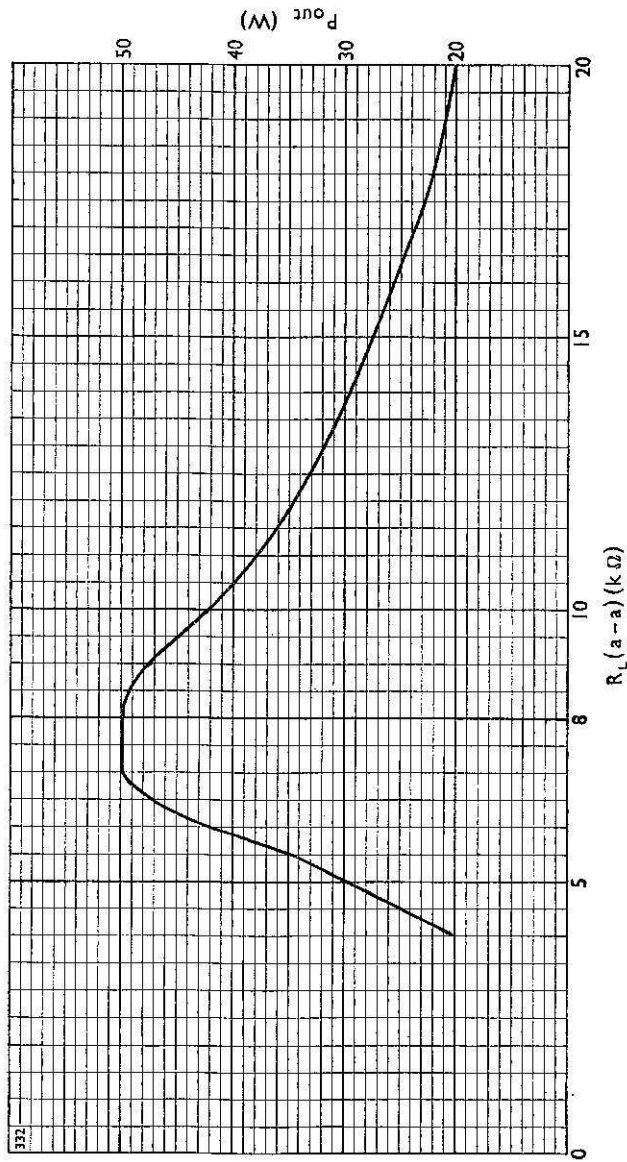


Fig. 8.